

# Edge detector

## SOLUTION

```
library ieee;
use ieee.std_logic_1164.all;
entity edge_detector1 is
    port(
        clk, reset: in std_logic;
        strobe: in std_logic;
        p1: out std_logic
    );
end edge_detector1;

architecture moore_arch of edge_detector1 is
    type state_type is (zero, edge, one);
    signal state_reg, state_next: state_type;
begin
    -- state register
    process(clk,reset)
    begin
        if (reset='1') then
            state_reg <= zero;
```

# Edge detector

## SOLUTION

```
    elsif (clk'event and clk='1') then
        state_reg <= state_next;
    end if;
end process;
-- next-state logic
process(state_reg, strobe)
begin
    case state_reg is
        when zero=>
            if strobe= '1' then
                state_next <= edge;
            else
                state_next <= zero;
            end if;
        when edge =>
            if strobe= '1' then
                state_next <= one;
            else
                state_next <= zero;
            end if;
        end case;
    end process;
```

# Edge detector

## SOLUTION

```
        end if;
    when one =>
        if strobe= '1' then
            state_next <= one;
        else
            state_next <= zero;
        end if;
    end case;
end process;
-- Moore output logic
p1 <= '1' when state_reg=edge else
    '0';
end moore_arch;
```

# Edge detector

## SOLUTION

- Machine d'états Moore sans la logique de sortie

```
architecture clever_assign_buf_arch of edge_detector1 is
    constant zero: std_logic_vector(1 downto 0) := "00";
    constant edge: std_logic_vector(1 downto 0) := "10";
    constant one: std_logic_vector(1 downto 0) := "01";
    signal state_reg, state_next: std_logic_vector(1 downto 0);
begin
    -- state register
    process(clk, reset)
    begin
        if (reset='1') then
            state_reg <= zero;
        elsif (clk'event and clk='1') then
            state_reg <= state_next;
        end if;
    end process;
    -- next-state logic
    process(state_reg, strobe)
```

# Edge detector

## SOLUTION

```
begin
  case state_reg is
    when zero=>
      if strobe= '1' then
        state_next <= edge;
      else
        state_next <= zero;
      end if;
    when edge =>
      if strobe= '1' then
        state_next <= one;
      else
        state_next <= zero;
      end if;
    when others =>
      if strobe= '1' then
        state_next <= one;
      else
        state_next <= zero;
```

# Edge detector

## SOLUTION

```
        end if;
    end case;
end process;
-- Moore output logic
p1 <= state_reg(1);
end clever_assign_buf_arch;
```

# Edge detector

## SOLUTION

- Machine d'états Moore avec la logique *look-ahead*

```
architecture look_ahead_arch of edge_detector1 is
    type state_type is (zero, edge, one);
    signal state_reg, state_next: state_type;
    signal p1_reg, p1_next: std_logic;
begin
    -- state register
    process(clk,reset)
    begin
        if (reset='1') then
            state_reg <= zero;
        elsif (clk'event and clk='1') then
            state_reg <= state_next;
        end if;
    end process;
    -- output buffer
    process(clk,reset)
    begin
```

# Edge detector

## SOLUTION

```
if (reset='1') then
    p1_reg <= '0';
elsif (clk'event and clk='1') then
    p1_reg <= p1_next;
end if;
end process;
-- next-state logic
process(state_reg, strobe)
begin
    case state_reg is
        when zero=>
            if strobe= '1' then
                state_next <= edge;
            else
                state_next <= zero;
            end if;
        when edge =>
            if strobe= '1' then
                state_next <= one;
```



# Edge detector

## SOLUTION


```
        else
            state_next <= zero;
        end if;
    when one =>
        if strobe= '1' then
            state_next <= one;
        else
            state_next <= zero;
        end if;
    end case;
end process;
-- look-ahead output logic
p1_next <= '1' when state_next=edge else
           '0';

-- output
p1 <= p1_reg;
end look_ahead_arch;
```

# EXEMPLE D'UTILISATION SUR LA CARTE
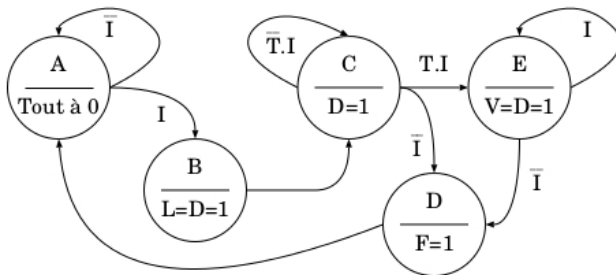
## BOUTON POUSOIR AUTOMATIQUE

On souhaite réaliser un système de comptage par bouton poussoir qui devient automatique (à 24Hz : division par  $2^{21}$  de l'horloge à 50MHz) si le bouton est maintenu plus de 1,34s (division par  $2^{26}$  de l'horloge à 50MHz)



# EXEMPLE D'UTILISATION SUR LA CARTE

## BOUTON POUSSOIR AUTOMATIQUE

